

Introduction to Chisel

Martin Schoeberl

Technical University of Denmark
Embedded Systems Engineering

September 9, 2025

Motivating Example:

Lipsi: Probably the Smallest Processor in the World

- ▶ Tiny processor
- ▶ Simple instruction set
- ▶ Shall be small
 - ▶ Around 200 logic cells, one FPGA memory block
- ▶ Hardware described in Chisel
- ▶ Available at <https://github.com/schoeberl/lipsi>
- ▶ Usage
 - ▶ Utility processor for small stuff
 - ▶ In teaching introduction to computer architecture
- ▶ The design took place on the island of Lipsi


The Design of Lipsi on Lipsi

Lipsi: a Minimalistic Microcontroller

Leros, Lipsi
16.7.2010 81

- Single on-chip memory \Rightarrow 2 cycles/instruction
- ≈ 200 Ld! (ld reg indirect is 3 cycles)
- 8 bit datapath, 8 bit variable length instructions
- Accu + 8 (16) register in memory
- 256 byte instructions, 256 byte data

Datapath:

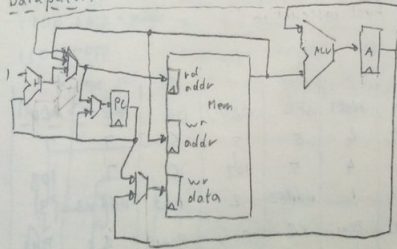

Lipsi Implementation

- ▶ Hardware described in Chisel
- ▶ Tester in Chisel/Scala
- ▶ Assembler in Scala
 - ▶ Core case statement about 20 lines
- ▶ Reference design of Lipsi as a software simulator in Scala
- ▶ Testing:
 - ▶ Self-testing assembler programs
 - ▶ Comparing hardware with a software simulator
- ▶ All in a single programming language!
- ▶ All in a single program
- ▶ How much work is this?

Chisel is Productive

- ▶ All coded and tested in less than 14 hours!
- ▶ The hardware in Chisel
- ▶ Assembler in Scala
- ▶ Some assembler programs (blinking LED)
- ▶ Simulation in Scala
- ▶ Two testers
- ▶ BUT, this does not include the design (done on paper)


Motivating Example: Lipsi, a Tiny Processor

- ▶ Show in IntelliJ

Chisel

- ▶ A hardware *construction* language
 - ▶ Constructing Hardware in a Scala Embedded Language
 - ▶ If it compiles, it is synthesizable hardware
 - ▶ Say goodbye to your unintended latches
- ▶ Chisel is not a high-level synthesis language
- ▶ Single source for two targets
 - ▶ Cycle accurate simulation (testing)
 - ▶ Verilog for synthesis
- ▶ Embedded in Scala
 - ▶ Full power of Scala available
 - ▶ We use Scala to write the generators
- ▶ Developed at UC Berkeley

The C Language Family

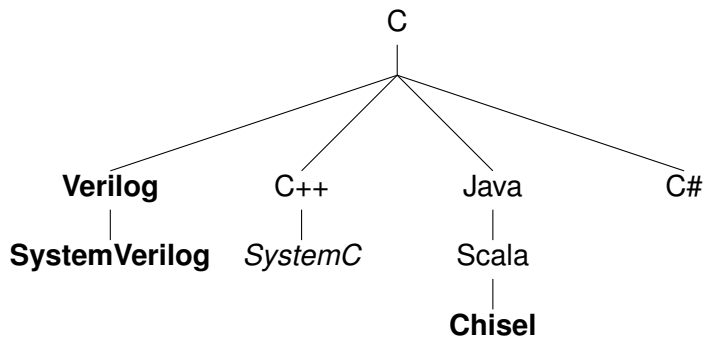

Other Language Families


Algol
|
Ada
|
VHDL

Python
|
MyHDL

A Small Language

- ▶ Chisel is a *small* language
- ▶ On purpose
- ▶ Not many constructs to remember
- ▶ The [Chisel Cheatsheet](#) fits on two pages
- ▶ The power comes with Scala for circuit generators
- ▶ With Scala, Chisel can grow with you


Tool Flow for Chisel Defined Hardware

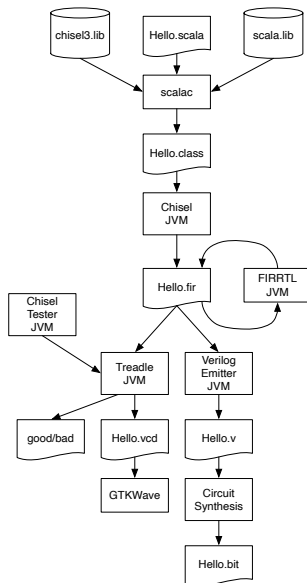

Chisel is a Hardware Construction Language

- ▶ The code looks much like Java code
- ▶ But it is *not* a program in the usual sense
- ▶ It represents a circuit
- ▶ The “program” constructs the circuit
- ▶ All statements are “executed” in parallel
- ▶ Statement order has *mostly* no meaning

A Chisel Book

 

- ▶ Available in open access ([as PDF](#))
 - ▶ Optimized for reading on a tablet (size, hyperlinks)
- ▶ Amazon can do the printout

Chisel and Scala

- ▶ Chisel is a library written in Scala
 - ▶ Import the library with `import chisel3._`
- ▶ Chisel code is Scala code
- ▶ When it is run is *generates* hardware
 - ▶ Verilog for synthesis and simulation
- ▶ Chisel is an embedded domain-specific language
- ▶ Two languages in one can be a little bit confusing

Chisel in Scala

- ▶ Chisel components are Scala classes
- ▶ Chisel code is in the constructor
- ▶ Executed at object creation time
- ▶ Builds the network of hardware objects
- ▶ Testers are written in Scala to drive the tests

Signal Types

- ▶ All types in hardware are a collection of bits
- ▶ The base type in Chisel is `Bits`
- ▶ `UInt` represents an unsigned integer
- ▶ `SInt` represents a signed integer (in two's complement)

`Bits(8.W)`

`UInt(8.W)`

`SInt(10.W)`

Number of Bits: $n.W$

- ▶ A collection of bits has a *width*
- ▶ The width is the number of bits
- ▶ Is written as number followed by $.W$
- ▶ Following example shows the width of n

$n.W$

`Bits($n.W$)`

Constants

- ▶ Constants can represent signed or unsigned numbers
- ▶ We use .U and .S to distinguish

```
0.U // defines a UInt constant of 0  
-3.S // defines a SInt constant of -3
```

- ▶ Constants can also be specified with a width

```
3.U(4.W) // An 4-bit constant of 3
```

Hexadecimal and Binary Representation

- ▶ We can specify constants with a different base
- ▶ May come handy sometimes

```
"hff".U           // hexadecimal representation of  
255  
"o377".U          // octal representation of 255  
"b1111_1111".U    // binary representation of 255
```

Boolean Values

- ▶ Type for logical values
- ▶ Can be true or false
- ▶ Almost exchangeable with `UInt(1.W)`
- ▶ Sometimes a signal, such as `valid`, may be better represented by a Boolean type


```
Bool()
```

```
true.B
```

```
false.B
```

Combinational Circuits

- ▶ Chisel uses Boolean operators, similar to C or Java
- ▶ `&` is the AND operator and `|` is the OR operator
- ▶ The following code is the same as the schematics
- ▶ `val logic` gives the circuit/expression the name `logic`
- ▶ That name can be used in following expressions

 

```
val logic = (a & b) | c
```

Combinational Circuits

- ▶ Simple expressions represent a circuit tree
- ▶ Arbitrary directed acyclic graphs need named subexpressions
- ▶ Using Scala's `val` keyword for variables that don't change
- ▶ Referenced multiple times

```
val cond = a & b  
val result = (cond & selA) | (!cond & selB)
```

Standard Logic Operations

```
val and = a & b // bitwise and  
val or  = a | b  // bitwise or  
val xor = a ^ b  // bitwise xor  
val not = ~a     // bitwise negation
```

- ▶ Note that we do not need to define the width of the values
- ▶ Note also that this is *hardware*
- ▶ All expressions are evaluated in parallel
- ▶ Order does not matter

Arithmetic Operations

- ▶ Same as in Java or C
- ▶ The width of the result is automatically computed
- ▶ E.g., the width of the multiplication is the sum of the width of a and the width of b

```
val add = a + b // addition
val sub = a - b // subtraction
val neg = -a    // negate
val mul = a * b // multiplication
val div = a / b // division
val mod = a % b // modulo operation
```


Comparison

- ▶ The usual operations (as in Java or C)
 - ▶ Unusual equal and unequal operator symbols
 - ▶ To keep the original Sala operators usable for references
- ▶ Operands are UInt and SInt
- ▶ Operands can be Bool for equal and unequal
- ▶ Result is Bool

>, >=, <, <=
==, !=

Boolean Logical Operations

- ▶ Operands and result are Bool
- ▶ Logical NOT, AND, and OR

```
val notX = !x  
val bothTrue = a && b  
val orVal = x || y
```

Chisel Defined Hardware Operators

Operator	Description	Data types
* / %	multiplication, division, modulus	UInt, SInt
+ -	addition, subtraction	UInt, SInt
=== !=	equal, not equal	UInt, SInt, returns Bool
> >= < <=	comparison	UInt, SInt, returns Bool
<< >>	shift left, shift right (sign extend on SInt)	UInt, SInt
~	NOT	UInt, SInt, Bool
& ^	AND, OR, XOR	UInt, SInt, Bool
!	logical NOT	Bool
&&	logical AND, OR	Bool

Wires

- ▶ A signal (or wire) can be first defined
- ▶ And later assigned an expression with `:=`

```
val w = Wire(UInt())
```

```
w := a & b
```

Connections

- ▶ Connections with the `:=` assignment
- ▶ When *reassigning* a value to a wire, port, or register

```
adder.io.a := ina  
adder.io.b := inb
```

Subfields and Concatenation

A single bit can be extracted as follows:

```
val sign = x(31)
```


A subfield can be extracted from end to start position:

```
val lowByte = largeWord(7, 0)
```

Bit fields are concatenated with the ## operator:

```
val word = highByte ## lowByte
```

A Multiplexer

 

- ▶ A Multiplexer selects between alternatives
- ▶ So common that Chisel provides a construct for it
- ▶ Selects `a` when `sel` is `true`. Otherwise `b`

```
val result = Mux(sel, a, b)
```

Combinational Circuit with Conditional Update

- ▶ Value first needs to be wrapped into a `Wire`
- ▶ Updates with the Chisel update operation `:=`
- ▶ With `when` we can express a conditional update
- ▶ The condition is an expression with a Boolean result
- ▶ The resulting circuit is a multiplexer
- ▶ The rule is that the last enabled assignment counts
 - ▶ Here the order of statements has a meaning

```
val enoughMoney = Wire(Bool())
```

```
enoughMoney := false.B  
when (coinSum >= price) {  
  enoughMoney := true.B  
}
```


The “Else” Branch

- ▶ We can express a form of “else”
- ▶ Note the `.` in `.otherwise`

```
val w = Wire(UInt())
```


```
when (cond) {  
  w := 1.U  
} .otherwise {  
  w := 2.U  
}
```

A Chain of Conditions

- ▶ To test for different conditions
- ▶ Select with a priority order
- ▶ The first that is true counts
- ▶ The hardware is a chain of multiplexers

```
val w = Wire(UInt())
```
 
```
when (cond) {  
  w := 1.U  
} .elsewhen (cond2) {  
  w := 2.U  
} .otherwise {  
  w := 3.U  
}
```



Default Assignment

- ▶ Practical for complex expressions
- ▶ Forgetting to assign a value at all conditions
 - ▶ Would describe a latch
 - ▶ Runtime error in Chisel
- ▶ Assign a default value is a good practice

```
val w = WireDefault(0.U)
```

```
when (cond) {  
  w := 3.U  
}
```

```
// ... and some more complex conditional  
  assignments
```

Logic Can Be Expressed as a Table

- ▶ Sometimes more convenient
- ▶ Still combinational logic (gates)
- ▶ Is converted to Boolean expressions
- ▶ Let the synthesis tool do the conversion!
- ▶ We use the `switch` statement

```
switch (sel) {  
  is ("b00".U) { result := "b0001".U}  
  is ("b01".U) { result := "b0010".U}  
  is ("b10".U) { result := "b0100".U}  
  is ("b11".U) { result := "b1000".U}  
}
```

The World of Combinational Logic

- ▶ With the shown operations (logic, arithmetic, Mux) all possible combinational circuits can be described
- ▶ Even the Mux is already *syntactic sugar*
 - ▶ A Mux is basically: $(a \ \& \ sel) \ | \ (b \ \& \ !sel)$
- ▶ But Chisel provides further constructs for more elegant description of circuits
- ▶ Stay tuned!

Lab 2


- ▶ Combinational circuits in Chisel
- ▶ [Chisel Lab 2 Page](#)
- ▶ Each exercise contains a test, which initially fails
- ▶ `sbt test` runs them all
 - ▶ To just run a single test, run e.g.,
`sbt "testOnly MajorityPrinter"`

When all test succeed you're done ;-)

- ▶ Components contain a comment where you shall add your implementation
- ▶ The initial majority example has an optional implementation in an FPGA


Sequential Building Blocks

 - ▶ Contain a register
- ▶ Plus combinational circuits



```
val q = RegNext(d)
```


Register With Reset

 

```
val valReg = RegInit(0.U(4.W))
```


```
valReg := inVal
```

 
Timing Diagram of the Register with Reset



- ▶ Also called waveform diagram
- ▶ Logic function over time
- ▶ Can be used to describe a circuit function
- ▶ Useful for debugging

Register with Enable

 

- Only when enable true is a value is stored

```
val enableReg = Reg(UInt(4.W))
```

```
when (enable) {  
    enableReg := inVal  
}
```

A Register with Reset and Enable


- ▶ We can combine initialization and enable

```
val resetEnableReg = RegInit(0.U(4.W))  
  
when (enable) {  
    resetEnableReg := inVal  
}
```

- ▶ A register can also be part of an expression
- ▶ What does the following circuit do?

```
val risingEdge = din & !RegNext(din)
```

A Register with an Adder is a Counter

 

- ▶ Is a free running counter
- ▶ 0, 1, ... 14, 15, 0, 1, ...

```
val cntReg = RegInit(0.U(4.W))
```

```
cntReg := cntReg + 1.U
```


A Counter with a Mux

```
val cntReg = RegInit(0.U(8.W))
```

```
cntReg := Mux(cntReg === 9.U, 0.U, cntReg + 1.U)
```

- ▶ This counter counts from 0 to 9
- ▶ And starts from 0 again after reaching 9
 - ▶ Starting from 0 is common in computer engineering
- ▶ A counter is the hardware version of a *for loop*
- ▶ Often needed

Counting Events

 

```
val cntEventsReg = RegInit(0.U(4.W))  
when(event) {  
    cntEventsReg := cntEventsReg + 1.U  
}
```

Counting Up and Down

► Up:

```
val cntReg = RegInit(0.U(8.W))
```

```
cntReg := cntReg + 1.U  
when(cntReg === N) {  
    cntReg := 0.U  
}
```

► Down:

```
val cntReg = RegInit(N)
```

```
cntReg := cntReg - 1.U  
when(cntReg === 0.U) {  
    cntReg := N  
}
```

Hello World in Chisel

```
class Hello extends Module {  
  val io = IO(new Bundle {  
    val led = Output(UInt(1.W))  
  })  
  val CNT_MAX = (500000000 / 2 - 1).U  
  
  val cntReg = RegInit(0.U(32.W))  
  val blkReg = RegInit(0.U(1.W))  
  
  cntReg := cntReg + 1.U  
  when(cntReg === CNT_MAX) {  
    cntReg := 0.U  
    blkReg := ~blkReg  
  }  
  io.led := blkReg  
}
```


Reminder: We Construct Hardware

- ▶ Chisel code looks much like Java code
- ▶ But it is *not* a program in the usual sense
- ▶ It represents a circuit
- ▶ We should be able to *draw* that circuit
- ▶ The “program” constructs the circuit
- ▶ All statements are “executed” in parallel
- ▶ Statement order has mostly no meaning

Structure With Bundles

- ▶ A Bundle to group signals
- ▶ Can be different types
- ▶ Defined by a class that extends Bundle
- ▶ Named fields as vals within the block
- ▶ Like a C struct or VHDL record

```
class Channel() extends Bundle {  
    val data = UInt(32.W)  
    val valid = Bool()  
}
```

Using a Bundle

- ▶ Create it with `new`
- ▶ Wrap it into a `Wire`
- ▶ Field access with *dot* notation

```
val ch = Wire(new Channel())  
ch.data := 123.U  
ch.valid := true.B  
  
val b = ch.valid
```

Wire, Reg, and IO

- ▶ `UInt`, `SInt`, and `Bits` are Chisel types, not hardware
- ▶ `Wire`, `Reg`, or `IO` generates hardware
 - ▶ A `Wire` is a combinational circuit
 - ▶ A `Reg` is a register
 - ▶ A `IO` is a connection/port (for a module)
- ▶ Can wrap any Chisel type, also `Bundle` or `Vec`
- ▶ Give it a name by assigning it to a `val`

```
val number = Wire(UInt())  
val reg = Reg(SInt())
```

Using = or :=

- ▶ Later assign or reassign a value or expression with :=

```
number := 10.U
```

```
reg := value - 3.U
```

- ▶ Note the small difference between = and :=
 - ▶ May be confusing to start with
- ▶ Use = when *creating* a hardware object to give it a name
- ▶ Use := when assigning or reassigning to an *existing* hardware object

Vectors

- ▶ Indexable vector of elements
- ▶ Elements can be Chisel basic elements, or bundles
- ▶ Type is specified as second parameter

```
val myVec = Vec(3, SInt(10.W))  
val y = myVec(2)  
myVec(0) := -3.S
```

- ▶ A register file as a register of a vector

```
val vecReg = Reg(Vec(32, SInt(32.W)))
```

Components/Modules


- ▶ Components/Modules are building blocks
 - ▶ Component and module are two names for the same thing
- ▶ Components have input and output ports (= pins)
 - ▶ Organized as a `Bundle`
 - ▶ Wrapped into an `IO()`
 - ▶ assigned to a field `io`
- ▶ We build circuits as a hierarchy of components
- ▶ In Chisel a component is called `Module`
- ▶ Components/Modules are used to organize the circuit
 - ▶ Similar to classes and methods in Java

Input/Output Ports

- ▶ Ports are the *interface* to a module
- ▶ Ports are bundles with directions
- ▶ Ports are used to connect modules

```
class AluIO extends Bundle {  
  val function = Input(UInt(2.W))  
  val inputA = Input(UInt(4.W))  
  val inputB = Input(UInt(4.W))  
  val result = Output(UInt(4.W))  
}
```


An Adder Module

 


- Practically too simple, but for the slides

An Adder Module

- ▶ A class that extends Module
- ▶ Interface (port) is a Bundle, wrapped into an IO(), and stored in the field io
- ▶ Circuit description in the constructor

```
class Adder extends Module {  
  val io = IO(new Bundle {  
    val a = Input(UInt(8.W))  
    val b = Input(UInt(8.W))  
    val y = Output(UInt(8.W))  
  })  
  
  io.y := io.a + io.b  
}
```

An Register Module

 


- ▶ Practically too simple, but for the slides

An Register Module

```
class Register extends Module {  
  val io = IO(new Bundle {  
    val d = Input(UInt(8.W))  
    val q = Output(UInt(8.W))  
  })  
  
  val reg = RegInit(0.U)  
  reg := io.d  
  io.q := reg  
}
```

An Counter out of Modules

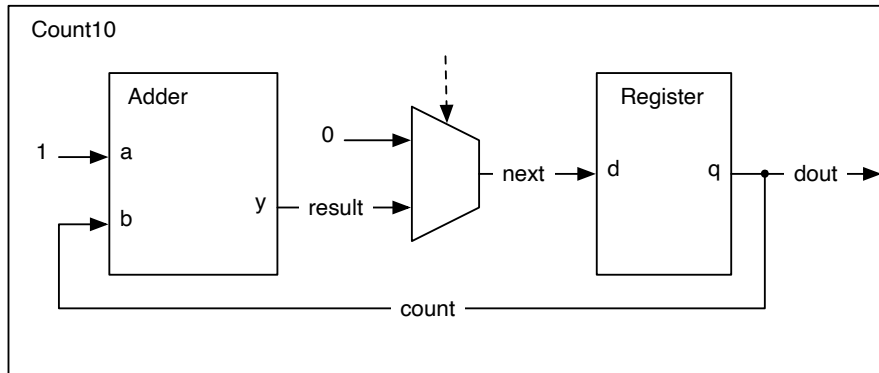

An Counter out of Modules

```
class Count10 extends Module {  
  val io = IO(new Bundle {  
    val dout = Output(UInt(8.W))  
  })  
  
  val add = Module(new Adder())  
  val reg = Module(new Register())  
  
  // the register output  
  val count = reg.io.q  
  // connect the adder  
  add.io.a := 1.U  
  add.io.b := count  
  val result = add.io.y  
  // connect the Mux and the register input  
  val next = Mux(count == 9.U, 0.U, result)  
  reg.io.d := next  
  io.dout := count  
}
```

Using Modules/Components

- ▶ Create with `new` and wrap into a `Module()`
- ▶ Interface port via the `io` field
- ▶ Note the assignment operator `:=` on `io` fields
- ▶ Note the dot access to the field `io` and then the IO field

Chisel Main

- ▶ Create one top-level Module
- ▶ Invoke the Chisel code emitter from the App
- ▶ Pass the top module (e.g., new Hello())
- ▶ Optional: pass some parameters (in an Array)
- ▶ Following code generates Verilog code for *Hello World*

```
object Hello extends App {  
  emitVerilog(new Hello())  
}
```


Testing with Chisel

- ▶ A test contains:
 - ▶ a device under test (DUT) and
 - ▶ the testing logic
- ▶ Set input values with `poke`
- ▶ Advance the simulation with `step`
- ▶ Read the output values with `peek`
- ▶ Compare the values with `expect`
- ▶ Import following packages:

```
import chisel3._  
import chiseltest._  
import org.scalatest.flatspec.AnyFlatSpec
```

An Example DUT

- ▶ A device-under test (DUT)
- ▶ Just 2-bit AND logic

```
class DeviceUnderTest extends Module {  
  val io = IO(new Bundle {  
    val a = Input(UInt(2.W))  
    val b = Input(UInt(2.W))  
    val out = Output(UInt(2.W))  
    val equ = Output(Bool())  
  })  
  
  io.out := io.a & io.b  
  io.equ := io.a === io.b  
}
```

A ChiselTest

- ▶ Extends class `AnyFlatSpec` with `ChiselScalatestTester`
- ▶ Has the device-under test (DUT) as parameter of the test function
- ▶ Test function contains the test code
- ▶ Testing code can use all features of Scala

A Test

- ▶ Poke values and expect some output

```
class SimpleTestExpect extends AnyFlatSpec
  with ChiselScalatestTester {
    "DUT" should "pass" in {
      test(new DeviceUnderTest) { dut =>
        dut.io.a.poke(0.U)
        dut.io.b.poke(1.U)
        dut.clock.step()
        dut.io.out.expect(0.U)
        dut.io.a.poke(3.U)
        dut.io.b.poke(2.U)
        dut.clock.step()
        dut.io.out.expect(2.U)
      }
    }
  }
}
```

Summary

- ▶ Chisel describes digital hardware embedded in Scala
- ▶ Digital design is simple: combinational circuits and registers
- ▶ We will make it more powerful with generator code
- ▶ A digital circuit is organized into components
- ▶ Components have ports with directions
- ▶ Sequential circuits are combinations of registers with combinational circuits

Lab 3

- ▶ Components and Small Sequential Circuits
- ▶ [Chisel Lab 3 Page](#)
- ▶ Each exercise contains a test, which initially fails
- ▶ `sbt test` runs them all
 - ▶ To just run a single test, run e.g.,
`sbt "testOnly SingleTest"`
- ▶ When all tests succeed, you're done ;-)